ExamGOAL
PYQ PDF

Free · With answer key

GATE ECE · ANALOG CIRCUITS · CHAPTER-WISE PYQS

555 Timer

GATE ECE Analog Circuits · Previous Year Questions with Answer Key

5	5	1997 – 2022	English
QUESTIONS	PAPERS COVERED	YEARS	LANGUAGE

INSIDE THIS PDF

Marks 1	2 questions
Marks 2	1 question
Marks 5	2 questions
Answer key	at the end

Practise online

Every question with its full solution, free on **questions.examside.com**


1. **Solve**
   Print it, or work through it on screen.
2. **Check**
   The answer key is on the last pages.
3. **Understand**
   Scan the QR code beside any question for its full solution.

Marks 1 2 questions

Q1. GATE ECE 2016 Set 3

In the astable multivibrator circuit shown in the figure, the frequency of oscillation (in kHz) at the output pin 3 is

Open solution

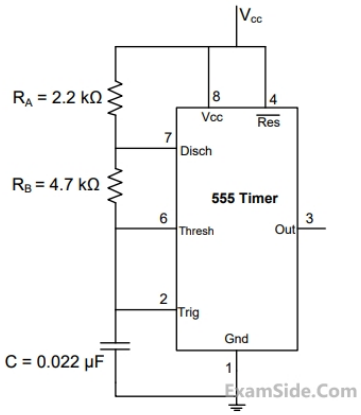

Q2. GATE ECE 2001

Consider the following two statements.

Statement 1: Astable Multivibrator can be used for generating Square Wave.

Statement 2: Bistable Multivibrator can be used for storing binary information.

Open solution

(A) only statement 1is correct

(B) only statement 2 is correct

(C) both the statement 1 and 2 are correct

(D) Both the statements 1 and 2 are in correct


Keep practising on the ExamGOAL app
Chapter-wise PYQs with solutions, full mock tests and analysis for JEE, NEET, GATE and more.
GET IT ON Google Play

Marks 2 1 questions

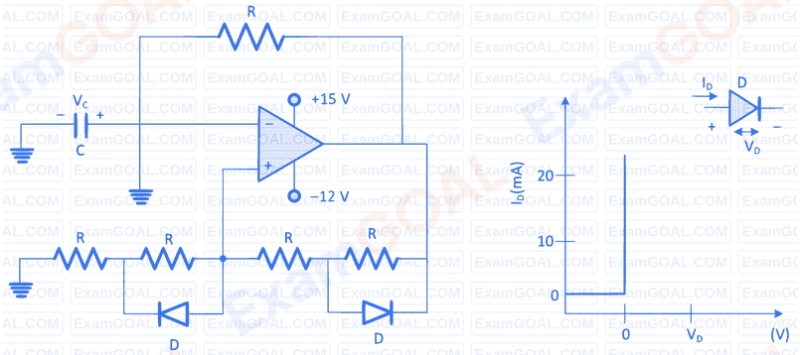Q3. GATE ECE 2022

Open solution

For the following circuit with an ideal OPAMP, the difference between the maximum and the minimum values of the capacitor voltage (V_C) is _____.




(A) 15 V (B) 27 V (C) 13 V (D) 14 V

Marks 5 2 questions

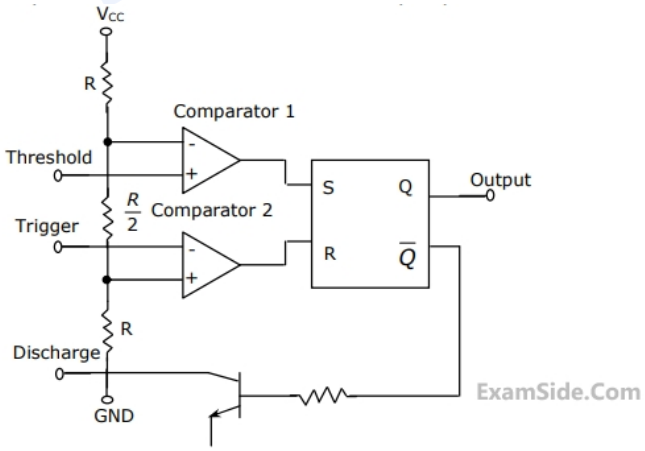Q4. GATE ECE 1998

Open solution

Implement a monostable multivibrator using the timer circuit shown, in Fig. Also determine an expression for ON time T of the o/p pulse.




Keep practising on the ExamGOAL app
Chapter-wise PYQs with solutions, full mock tests and analysis for JEE, NEET, GATE and more.
GET IT ON Google Play

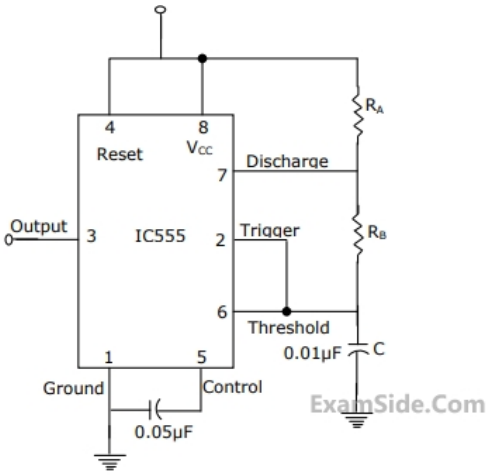Q5. GATE ECE 1997

Open solution

An IC 555 chip has been used to construct a pulse generator. Typical pin connections with components is shown below in fig. for such application. However it is desired to generate a square pulse of 10KHz..



Evaluate values of R_A and R_B and if the capacitor has the value of 0.01μF for the configuration closed. If necessary you can suggest modifications in the external circuit configuration.

Keep practising on the ExamGOAL app
Chapter-wise PYQs with solutions, full mock tests and analysis for JEE, NEET, GATE and more.
GET IT ON Google Play

Answer Key

Marks 1

1. **5.65**	2. **C**

Marks 2

3. **C**

Marks 5

4. **TON = 0.916**$R_A C_A$	5. R_A **=** R_B **= 7.10 KΩ**

For numerical answers given as a range, any value within the range is correct. Full solutions: scan the QR code next to each question, or visit questions.examside.com.

Keep practising on the ExamGOAL app
Chapter-wise PYQs with solutions, full mock tests and analysis for JEE, NEET, GATE and more.
GET IT ON Google Play

ExamGOAL
PYQ PDF

Your Exam. Our Responsibility.

From first chapter to exam day.

Practise with the questions your exam has already asked, then test yourself under real exam conditions.

PAST YEAR QUESTIONS

Every past paper, chapter-wise.

Previous year questions sorted the way you study, each with a full solution.

- Chapter-wise and year-wise
- Weightage and topic tags on every chapter
- Your progress on each one, at a glance

MOCK TESTS

Mock tests with a real exam feel.

Practise under the same pressure as the real paper, on your phone or on the big screen.

- Timed sections, just like exam day
- Mark questions for review and come back

ANALYSIS

Know your score. Know your rank.

A full report after every test, so you know exactly where you stand.

- Your percentile among everyone who took it
- Predicted real-exam percentile and All India Rank
- Subject breakdown and time analysis

PRACTICE

Solve. Check. Understand.

Learn from every question, not just the ones you get right.

- Instant answers as you practise
- Step-by-step explanations
- See how everyone else answered

NCERT Exemplar
With full solutions

Exam syllabus
Subject and chapter-wise

Bookmarks
Organised in groups

Your notes
On any question

ExamGOAL
LEARNING APP

ExamGOAL: Exam Preparation App

One app for every exam. Free trial for new users, on Android and the web.

GET IT ON Google Play

Scan to get the app

www.examgoal.com
Practice and mock tests

questions.examside.com
Free solutions

pdf.questions.examgoal.com
Free PYQ PDFs