ExamGOAL
PYQ PDF

Free · With answer key

GATE ECE · NETWORK THEORY · CHAPTER-WISE PYQS

Miscellaneous

GATE ECE Network Theory · Previous Year Questions with Answer Key

4	3	1991 – 2000	English
QUESTIONS	PAPERS COVERED	YEARS	LANGUAGE

INSIDE THIS PDF

Marks 2	2 questions
Marks 3	1 question
Marks 5	1 question
Answer key	at the end

Practise online

Every question with its full solution, free on **questions.examside.com**


1. **Solve**
   Print it, or work through it on screen.
2. **Check**
   The answer key is on the last pages.
3. **Understand**
   Scan the QR code beside any question for its full solution.

Marks 2 2 questions

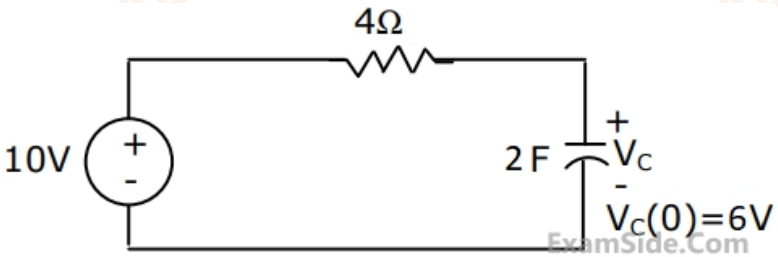Q1. GATE ECE 1997

Open solution

In the circuit of Fig., energy absorbed by the 4 Ω registor in the time interval $(0,\infty)$ is



(A) 36 Joules
(B) 16 Joules
(C) 256 Joules
(D) None of the above

Q2. GATE ECE 1991

Open solution

The necessary and sufficient condition for a rational function of s, T(s) to be driving point impedance of an RC network is that all poles and zeros should be


(A) simple and lie on the negative axis in the s-plane
(B) complex and lie in the left half of the s-plane
(C) complex and lie in the right half of the s-plane
(D) simple and lie on the positive real axis of the s-plane

Marks 3 1 questions

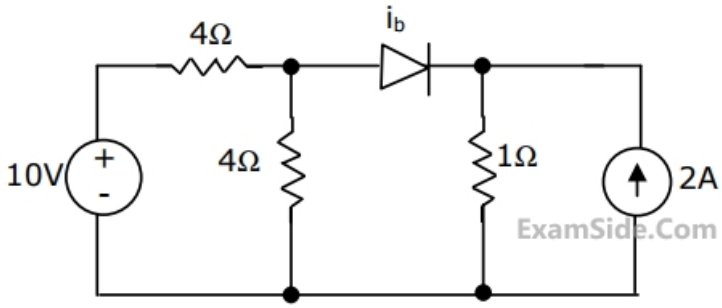Q3. GATE ECE 1997

Open solution

In the circuit of Fig., the current i_D through the ideal diode (zero cut in voltage and zero forward resistance) equals



(A) 0 A
(B) 4 A
(C) 1 A
(D) None of the above


Keep practising on the ExamGOAL app
Chapter-wise PYQs with solutions, full mock tests and analysis for JEE, NEET, GATE and more.
GET IT ON Google Play

Marks 5 1 questions

Q4. GATE ECE 2000

Open solution

For the circuit in Fig.

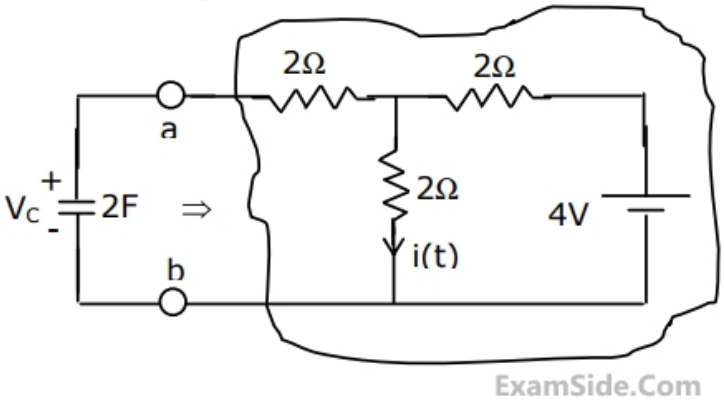

(a) Find the Thevenin equivalent of the sub circuit faced by the capacitor across the terminals a, b.

(b) Find $v_c(t),\ t > 0,\ given\ v_c(0) = 0$.

(c) Find i(t), t>0.

Keep practising on the ExamGOAL app
Chapter-wise PYQs with solutions, full mock tests and analysis for JEE, NEET, GATE and more.
GET IT ON Google Play

Answer Key

Marks 2

1. **B**	2. **A**

Marks 3

3. **C**

Marks 5

4. **Solve it.**

For numerical answers given as a range, any value within the range is correct. Full solutions: scan the QR code next to each question, or visit questions.examside.com.

Keep practising on the ExamGOAL app
Chapter-wise PYQs with solutions, full mock tests and analysis for JEE, NEET, GATE and more.
GET IT ON Google Play

ExamGOAL
PYQ PDF

Your Exam. Our Responsibility.

From first chapter to exam day.

Practise with the questions your exam has already asked, then test yourself under real exam conditions.

PAST YEAR QUESTIONS

Every past paper, chapter-wise.

Previous year questions sorted the way you study, each with a full solution.

- Chapter-wise and year-wise
- Weightage and topic tags on every chapter
- Your progress on each one, at a glance

MOCK TESTS

Mock tests with a real exam feel.

Practise under the same pressure as the real paper, on your phone or on the big screen.

- Timed sections, just like exam day
- Mark questions for review and come back

ANALYSIS

Know your score. Know your rank.

A full report after every test, so you know exactly where you stand.

- Your percentile among everyone who took it
- Predicted real-exam percentile and All India Rank
- Subject breakdown and time analysis

PRACTICE

Solve. Check. Understand.

Learn from every question, not just the ones you get right.

- Instant answers as you practise
- Step-by-step explanations
- See how everyone else answered

NCERT Exemplar
With full solutions

Exam syllabus
Subject and chapter-wise

Bookmarks
Organised in groups

Your notes
On any question

ExamGOAL
LEARNING APP

ExamGOAL: Exam Preparation App

One app for every exam. Free trial for new users, on Android and the web.

GET IT ON Google Play

Scan to get the app

www.examgoal.com
Practice and mock tests

questions.examside.com
Free solutions

pdf.questions.examgoal.com
Free PYQ PDFs