ExamGOAL
PYQ PDF

Free · With answer key

GATE ECE · ANALOG CIRCUITS · CHAPTER-WISE PYQS

Power Amplifier

GATE ECE Analog Circuits · Previous Year Questions with Answer Key

9	7	1987 – 2006	English
QUESTIONS	PAPERS COVERED	YEARS	LANGUAGE

INSIDE THIS PDF

Marks 1	6 questions
Marks 2	3 questions
Answer key	at the end

Practise online

Every question with its full solution, free on **questions.examside.com**

1. **Solve**
   Print it, or work through it on screen.
2. **Check**
   The answer key is on the last pages.
3. **Understand**
   Scan the QR code beside any question for its full solution.

Marks 1 6 questions

Q1. GATE ECE 2005

The effect of current shunt feedback in an amplifier is to

(A) increase the input resistance and decrease the output resistance

(B) increase both input and output resistances

(C) decrease both input and output resistances

(D) decrease the input resistances and increase the output resistance.

Open solution

Q2. GATE ECE 1999

Crossover distortion behavior is characteristic of

(A) class A output stage

(B) class B output stage


(C) class AB output stage

(D) common- base output stage

Open solution

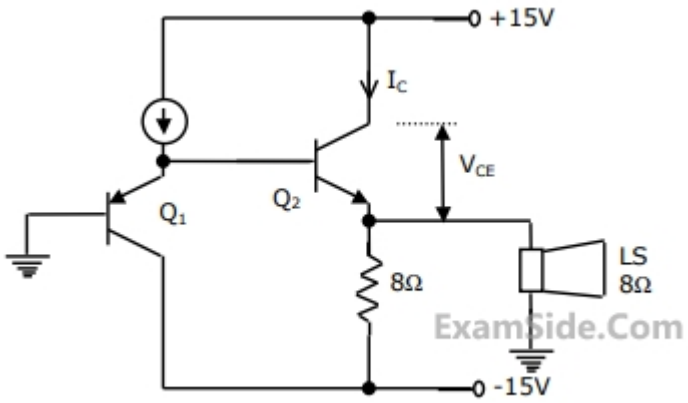Q3. GATE ECE 1995

The circuit shown, the figure supplies power to on 8 v speaker or L.S. The vaLUES OF I_C and V_{CE} for this ciruit will be



Open solution

Q4. GATE ECE 1995

A power Amplifier delivers 50 W output at 50% efficiency. The ambient temperature is 25° C. if the maximum allowable junction temperature is 150 ° C, then the maximum thermal resistance θ_{Jc} that can be tolerated is

Open solution

Q5. GATE ECE 1994

A class-A transformer coupled, transistor power Amplifier is required to deliver a power rating of the transistor should not be less than.

(A) 5 W

(B) 10 W

(C) 20 W

(D) 40 W

Open solution

Keep practising on the ExamGOAL app
Chapter-wise PYQs with solutions, full mock tests and analysis for JEE, NEET, GATE and more.
GET IT ON Google Play

Q6. GATE ECE 1993

In a transistor push-pull Amplifier

(A) there is no d.c present in the o/p.

(B) there is no distortion in the o/p.

(C) there is no even harmonics in the o/p.

(D) there is no odd harmonics in the o/p.


Open solution

Marks 2 3 questions

Q7. GATE ECE 2006

A regulated power supply, shown in figure below, has an unregulated input (UR) of 15 volts and generates a regulated output $V_{out.}$ .Use the component values shown in the figure.

Open solution

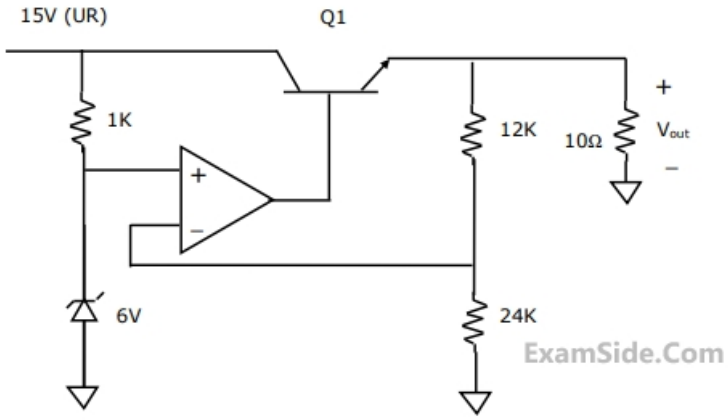

The power dissipation across the transistor Q1 shown in the figure is

(A) 4.8 Watts

(B) 5.0 Watts

(C) 5.4 Watts


(D) 6.0 Watts

Keep practising on the ExamGOAL app
Chapter-wise PYQs with solutions, full mock tests and analysis for JEE, NEET, GATE and more.
GET IT ON Google Play

Q8. GATE ECE 2006

A regulated power supply, shown in figure below, has an unregulated input (UR) of 15 volts and generates a regulated output V o u t . out. .Use the component values shown in the figure.

Open solution

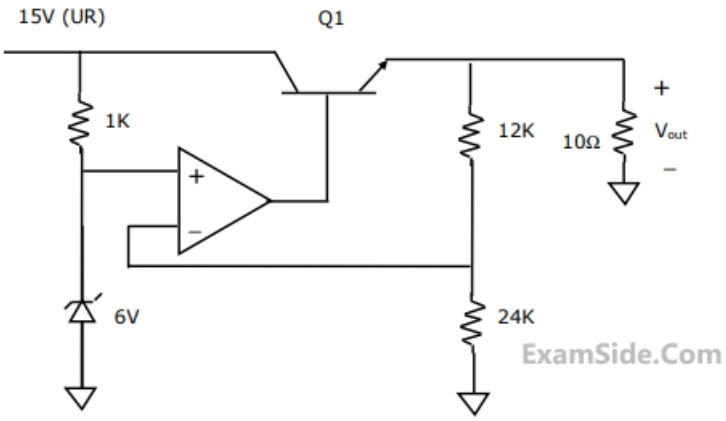

If the unregulated voltage increases by 20% the power dissipation across the transistor Q_1

(A) increases by 20%
(B) increases by 50%
(C) remains unchanged
(D) decreases by 20%

Q9. GATE ECE 1987

In case of class A amplifiers, the ratio (efficiency of transformer coupled amplifier)/(efficiency of a transformer less amplifier) is

(A) 2.9
(B) 2
(C) 1.0
(D) 0.5

Open solution

Keep practising on the ExamGOAL app
Chapter-wise PYQs with solutions, full mock tests and analysis for JEE, NEET, GATE and more.
GET IT ON Google Play

Answer Key

Marks 1

1. **D**	2. **B**	3. **15 V**	4. **2.5° C /W**	5. **B**
6. **A, C**				

Marks 2

7. **B**	8. **D**	9. **B**

For numerical answers given as a range, any value within the range is correct. Full solutions: scan the QR code next to each question, or visit questions.examside.com.

Keep practising on the ExamGOAL app
Chapter-wise PYQs with solutions, full mock tests and analysis for JEE, NEET, GATE and more.
GET IT ON Google Play

ExamGOAL
PYQ PDF

Your Exam. Our Responsibility.

From first chapter to exam day.

Practise with the questions your exam has already asked, then test yourself under real exam conditions.

PAST YEAR QUESTIONS

Every past paper, chapter-wise.

Previous year questions sorted the way you study, each with a full solution.

- Chapter-wise and year-wise
- Weightage and topic tags on every chapter
- Your progress on each one, at a glance

MOCK TESTS

Mock tests with a real exam feel.

Practise under the same pressure as the real paper, on your phone or on the big screen.

- Timed sections, just like exam day
- Mark questions for review and come back

ANALYSIS

Know your score. Know your rank.

A full report after every test, so you know exactly where you stand.

- Your percentile among everyone who took it
- Predicted real-exam percentile and All India Rank
- Subject breakdown and time analysis

PRACTICE

Solve. Check. Understand.

Learn from every question, not just the ones you get right.

- Instant answers as you practise
- Step-by-step explanations
- See how everyone else answered

NCERT Exemplar
With full solutions

Exam syllabus
Subject and chapter-wise

Bookmarks
Organised in groups

Your notes
On any question

ExamGOAL
LEARNING APP

ExamGOAL: Exam Preparation App

One app for every exam. Free trial for new users, on Android and the web.

GET IT ON Google Play

Scan to get the app

www.examgoal.com
Practice and mock tests

questions.examside.com
Free solutions

pdf.questions.examgoal.com
Free PYQ PDFs